

# DD Project: Digital Safe

---

Rishabh Acharya, Ayush Pekamwar, Pujit Jha

# Features


1. Different LEDs for different states
2. Ability to set new password (only when in the logged-in state)
3. Permanent locking of the device on 3 incorrect attempts
4. An external 7 segment display which shows the current state of the device
5. Option to reset the entered input
6. Countdown of the number of incorrect inputs

# Concept


## Finite State Machine

```
//parameters are the binary numbers chosen for different states  
parameter[3:0] init_state = 4'b0000 , logout = 4'b0110 , login = 4'b0101 , locked = 4'b1011;  
parameter[3:0] num1 = 4'b0001 , num2 = 4'b0010 , num3 = 4'b0011 , num4 = 4'b0100;  
parameter[3:0] entered_num1 = 4'b0111 , entered_num2 = 4'b1000 , entered_num3 = 4'b1001 , entered_num4 = 4'b1010;
```

# State Transition Diagram

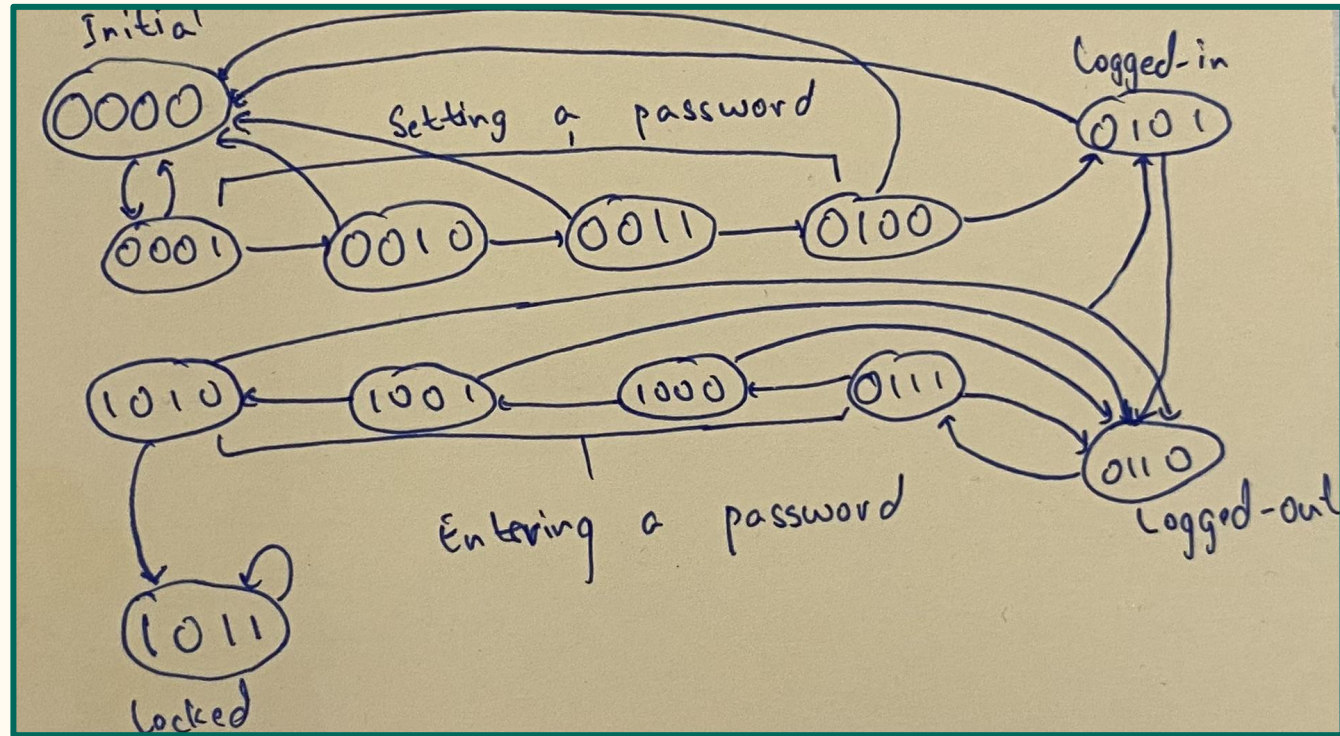

# Simulation

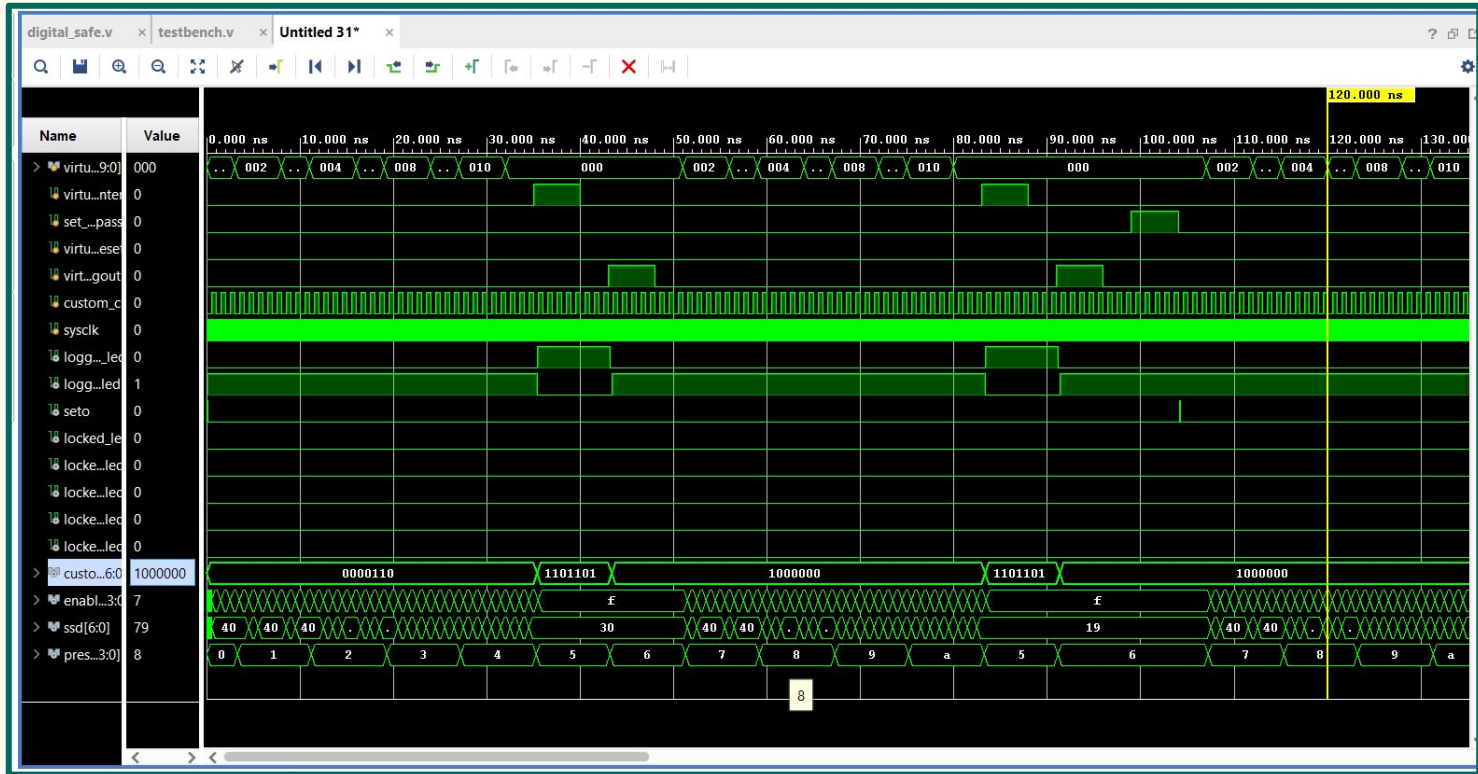

**NOTE:** This is a snippet of the simulation as it is too big to fit inside one screenshot

# Important Aspects

1. Clock frequency reduced for better visualization
2. Implementation of virtual button module to store previous high state on positive edge of clock; prevents overwriting on other SSDs
3. No transitions from locked state, signifying that no further changes can be made to the device
4. Displays on external SSD:
  - a. Initial state: 'I'
  - b. Logged-in state: 'S'
  - c. Logged-out state: '-'
  - d. Countdown of number of incorrect attempts available: '2' / '1'
  - e. Locked state: 'F'

# Contributions

Virtual button module and concept: Rishabh

State designing and code ideation: Pujit, Ayush

Testbench and simulation: Rishabh

Implementation: Rishabh, Ayush, Pujit